




Source Follower and Differential Pair



The Source Follower (Common Drain Stage, SF)

- Current source I_0 pulls a constant current through the MOS
- This fixes V_{GS} of M1 (to $V_T + \text{Sqrt}(\dots)$)
- Therefore, $V_{in} - V_{out} = V_{GS}$ is *nearly* constant (see later)
- The small signal gain is close to 1

 
$$V_{out} \sim V_{in} - \text{constant} \rightarrow v_{out} \sim v_{in} \rightarrow g = v_{out}/v_{in} \sim 1$$





Simulation

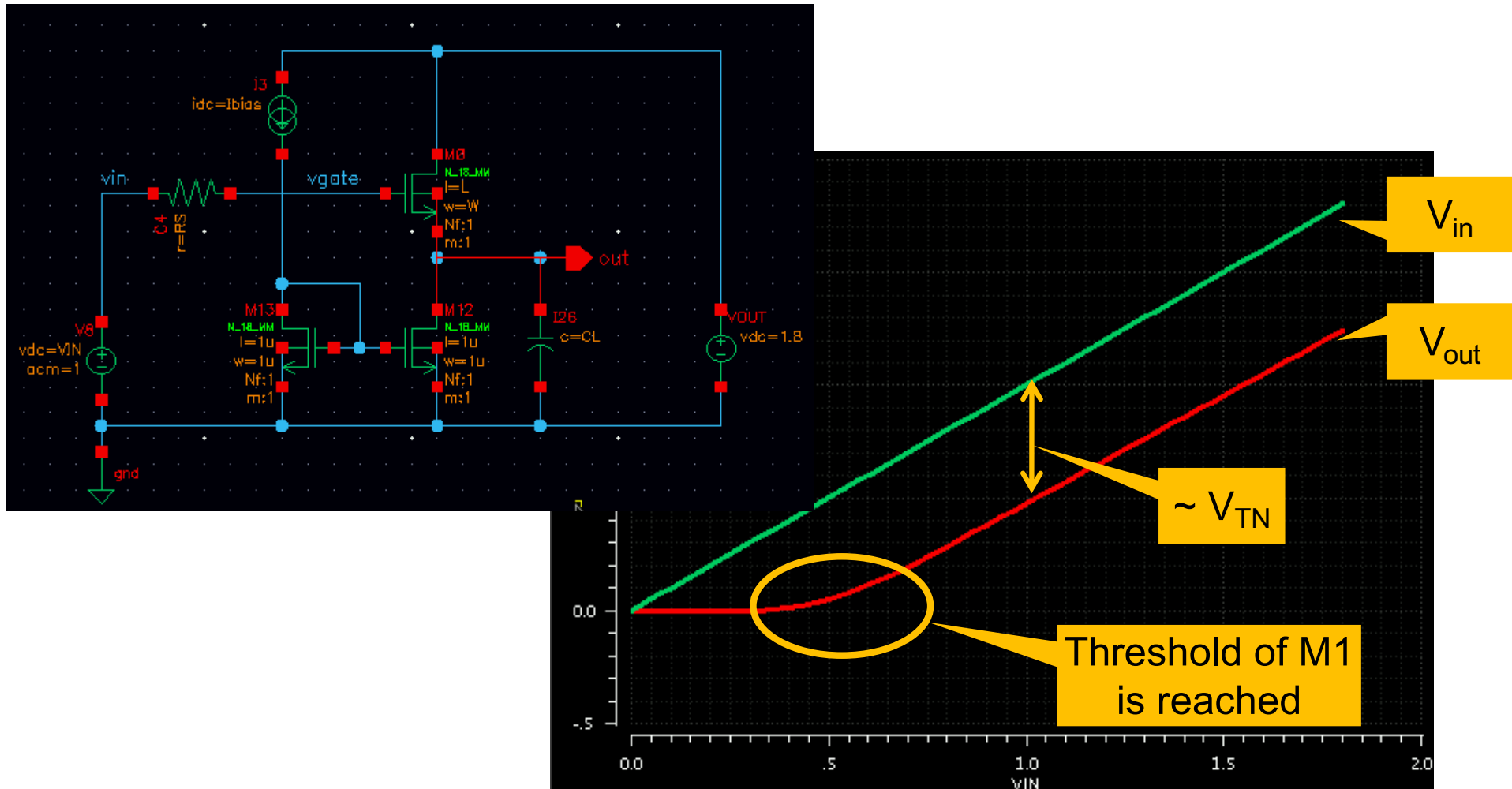- NMOS Source Follower with NMOS current source:
 - Starts to work when $V_{in} > V_{T,NMOS} + V_{DSat,Source}$






Real Source Follower (Here *with* substrate effect)

- In reality, we must consider
 - r_{ds} of M1 and of current source
 - body effect (if $V_B \neq V_S$)

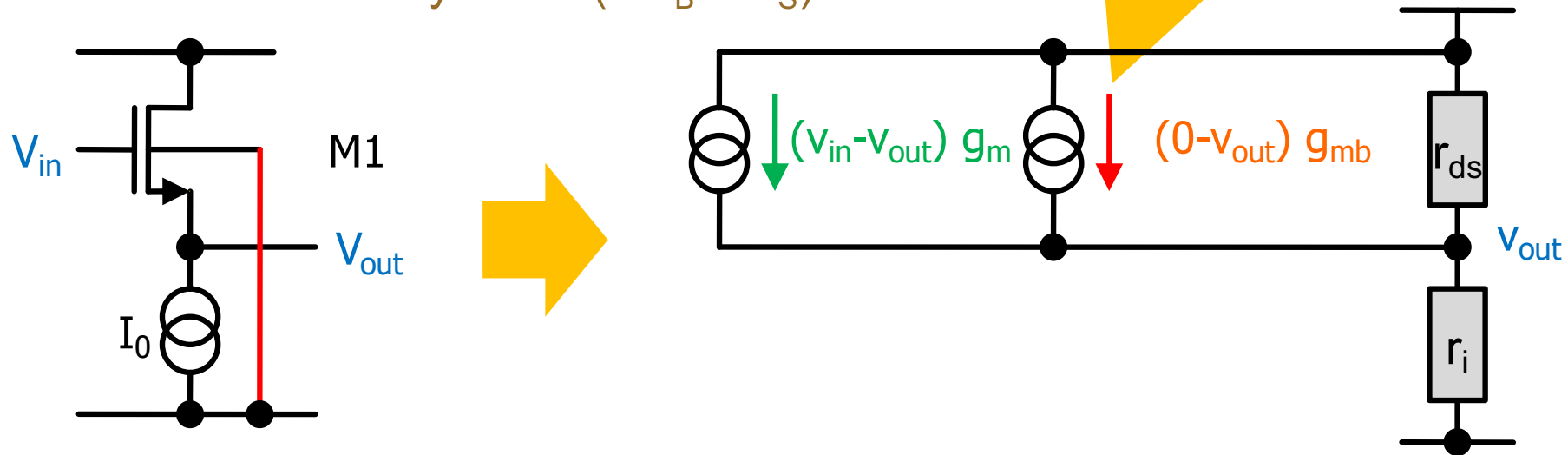body effect (if body = ground):
 $i = v_{BS} g_{mb}$



▪
$$\text{gain} = \frac{g_m r_{ds} r_i}{r_{ds} + r_i + g_m r_{ds} r_i + g_{mb} r_{ds} r_i} = \frac{g_m}{g_{ds} + g_i + g_m + g_{mb}} \sim \frac{g_m}{g_m + g_{mb} + g_{ds}}$$

with $g_{ds} = 1 / r_{ds}$, $g_i = 1/r_i$ and $g_{ds} \ll g_m \dots$

- Gain is *always* ≤ 1 . With $g_{mb} = (n-1) g_m$, gain $\sim 1/n \sim 0.7$



Source Follower with $g=1$?

- From $g = \frac{g_m}{g_{ds} + g_i + g_m + g_{mb}}$ we see that we approach $g=1$ with
 - $g_{mb} = 0 \rightarrow$ connect bulk an source of M1. This is often not possible for NMOS (bulk = substrate = ground)
 - $g_i = 0 \rightarrow$ Make a good current source:
 - long MOS
 - Cascode, ...
 This will lead to higher V_{DSat} so that SF works ‚later‘
 - $g_{ds} = 0 \rightarrow$ Hard.
 - Longer MOS helps, but g_m suffers (ratio does not increase quickly, speed suffers)
 - Cascode not possible because we change source!

- Reaching an *exact* gain of 1 is not really possible!


- Obvious: If a SF is loaded by a *resistive* load, gain drops!



Advanced: Source Follower with finite source imp.

For instance
a gain stage

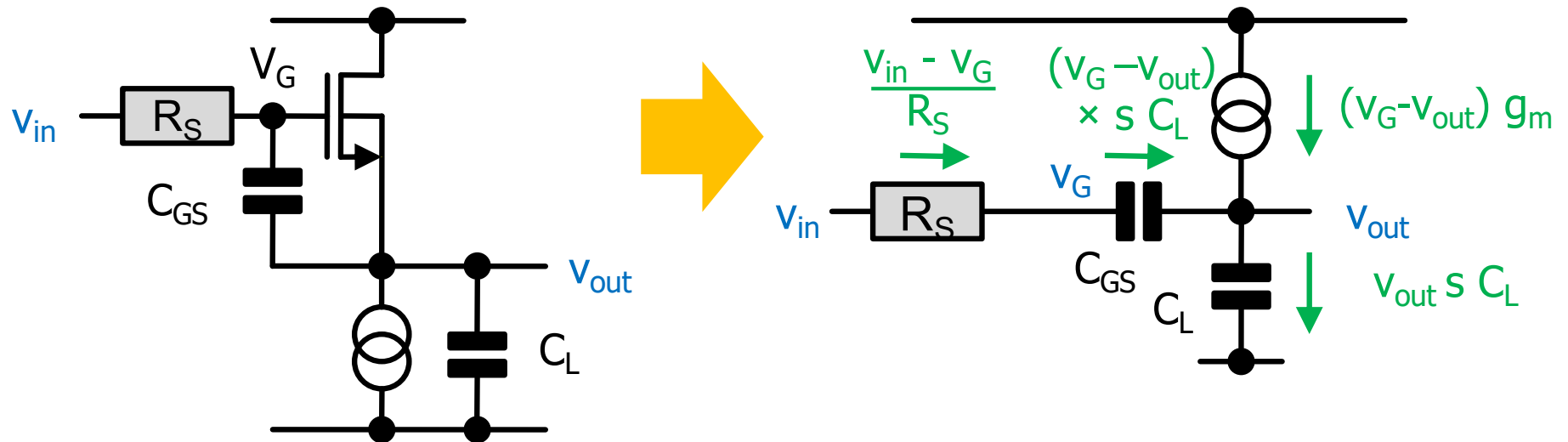- Consider the case when the SF is driven by a 'high impedance' source (with output resistance R_S):
 - Take into account the Gate-Source cap. C_{GS} and output cap. C_L
 - neglect output impedances and g_{mb} for simplicity...



- The transfer function has *two* poles:



$$\frac{g_m + C_{gs} s}{g_m + s(C_{gs} + C_L + C_{gs} C_L r_s)}$$

- There is an *Overshoot* as soon as $R_S > \frac{(C_{gs} + C_L)^2}{4 C_{gs} C_L g_m}$



Simulation

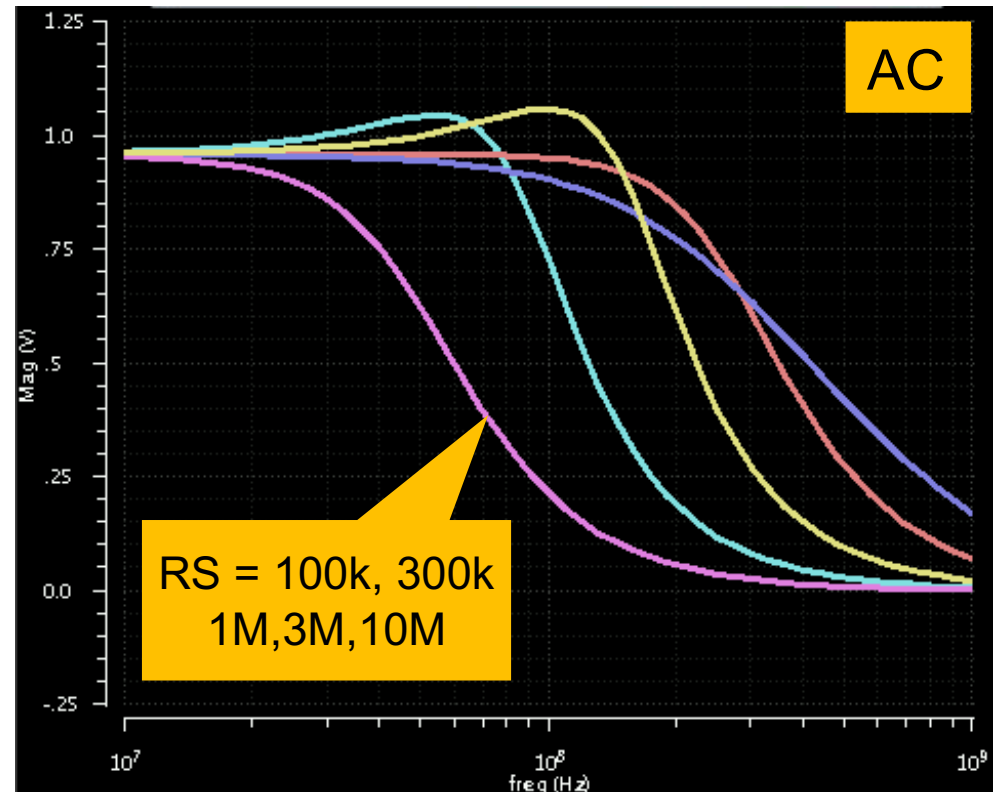 - 180nm Technology, $W/L = 1\mu/0.18\mu$, $C_L = 100\text{fF}$, $I_{\text{bias}} = 10\mu\text{A}$




- Therefore remember:
Source Followers driving capacitive loads are *dangerous!*



What for?

 
- The Source Follower has a low output impedance ($1/g_m$)
- It can 'drive' low-impedance loads
- Gain drops 'only a bit'
 - (gain of a gain stage drops 'a lot' with resistive loads)
- Often used in combination with a gain stage:





Special Application

 - SF be used to ,send' a voltage
- Multiple Source Followers can be combined:



Enable only one ,channel' at a time

Switches can be NMOS (on output side)





THE DIFFERENTIAL PAIR



The (Differential) Pair

  - Very often, the *difference* of voltages must be amplified
- The basic circuit are two MOS with ***connected sources***:



- Assume $V_+ = V_-$
 - $\rightarrow V_{GS, \text{left}} = V_{GS, \text{right}} \rightarrow I_+ = I_- = I_0 / 2$
- Assume $V_+ > V_-$
 - $\rightarrow V_{GS, \text{left}} > V_{GS, \text{right}}$
 - $\rightarrow I_+ > I_-$
- Assume $V_+ \gg V_- \rightarrow I_+ \sim I_0, I_- \sim 0$



What is V_S ?

- V_S is (roughly) one threshold voltage below the **higher** input voltage
- It is often called the ‘tail’ voltage V_{tail} .
- The pair only works for input voltages $> V_{\text{TH}}$
- The tail current is normally provided by a current source which needs additional (saturation) voltage headroom




The Switching Voltage in *Strong* Inversion

- We have $I_D[VGS_] = \beta (VGS - V_{TH})^2$; with $\beta = K/2 W/L$
- We have 3 equations for 3 unknowns (I_P , I_N , V_S):

$$I_P == I_D[V_P - V_S];$$

$$I_N == I_D[V_N - V_S];$$


$$I_P + I_N == I_0;$$

 

- We get $I_P = \frac{1}{2} \left(I_0 + \sqrt{\beta \Delta V^2 (2 I_0 - \beta \Delta V^2)} \right)$ with $\Delta V = V_P - V_N$

- We switch **completely** for
 
$$\Delta V_{SW} = \frac{\sqrt{I_0}}{\sqrt{\beta}}$$




- Conclusion: In *strong inversion*, pair can be *fully* switched!



The Switching Voltage in *Weak* Inversion

 - We have $I_D[VGS_] = \beta \text{Exp}\left[\frac{VGS}{n UT}\right]$;
- We get $I_P = \frac{I_0}{1 + e^{\frac{\Delta V}{n UT}}}$ with $\Delta V = V_P - V_N$ and $UT = 25.6 \text{ mV}$
- We switch in a few UT , but **never** switch 'really' completely




- Conclusion: In *weak inversion*, pair switches at *small voltages*, but never fully!



The Differential Amplifier


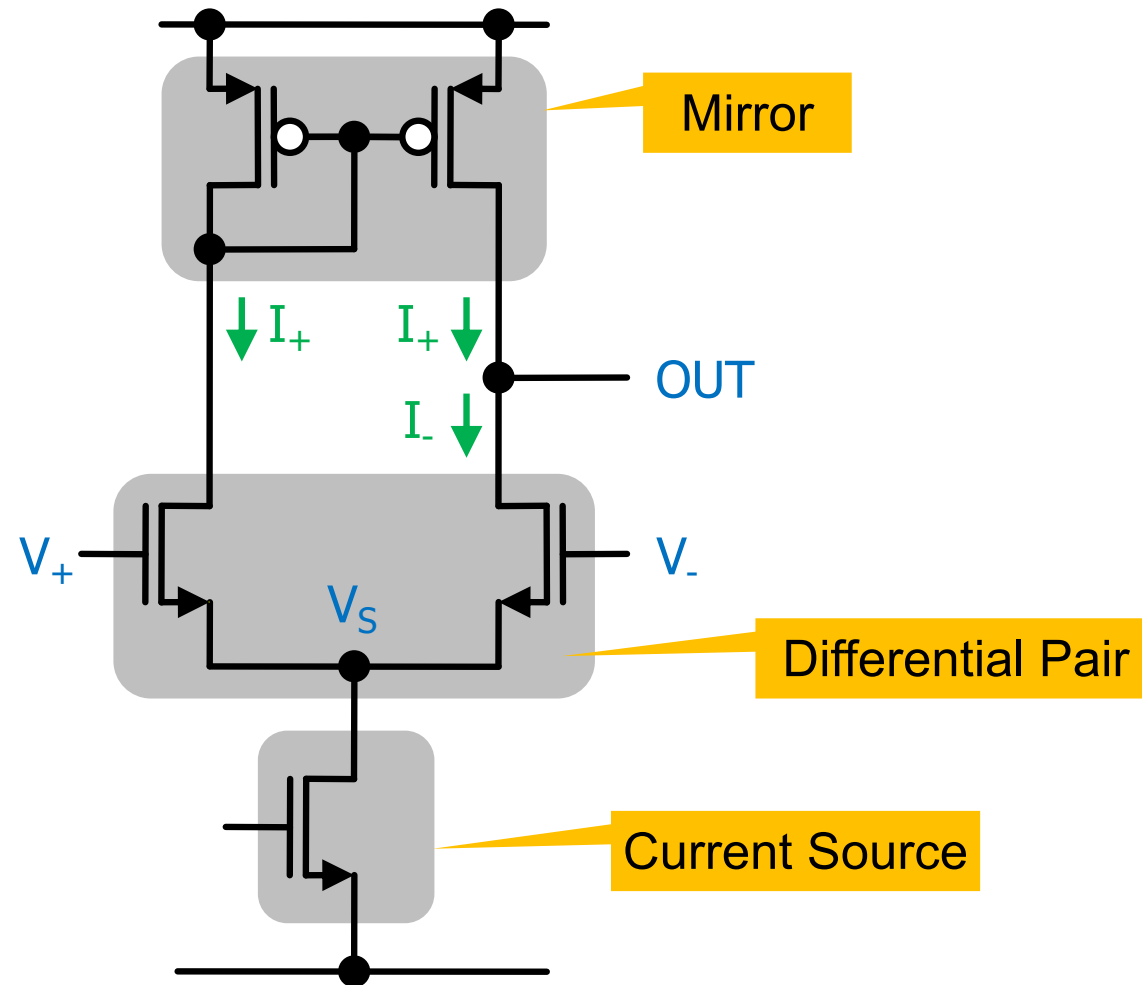
- One 'output' current is often mirrored and added to the other:





Output *Current* of the Differential Amplifier

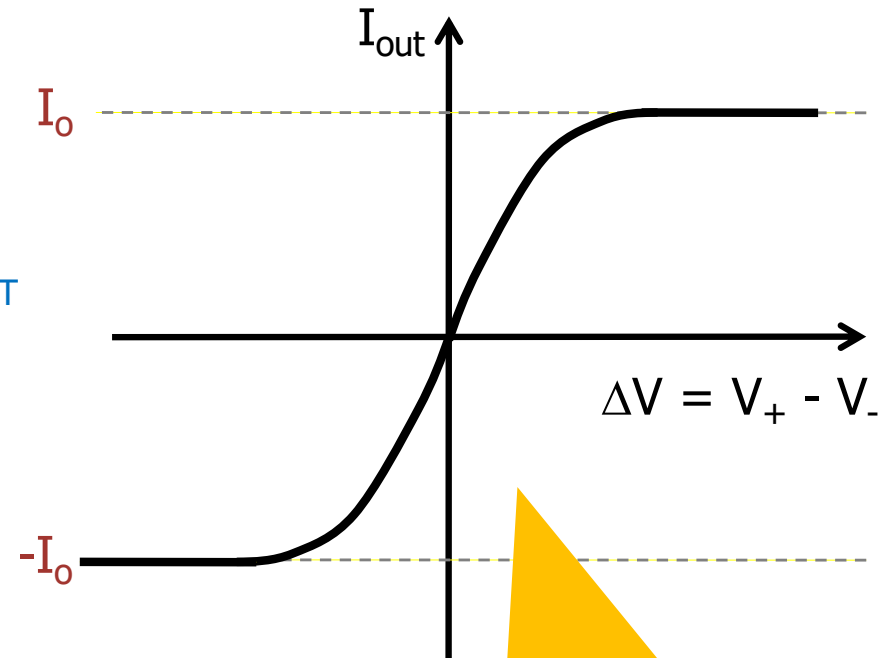 - If the output voltage is *fixed*, the *output current* is just $I_+ - I_-$
- The circuit is a ‚*Transconductor*‘ (it converts $\Delta U \rightarrow I$)





This only works if the V_{OUT} is ‚good‘
... understand what this means! ...



Output *Voltage* of the Differential Amplifier

  - If *no current* flows out of the circuit and the output voltage is left free, we have *voltage* gain (the current pulls V_{out} hi/low)




Output cannot go lower than $V_S \sim V_+ - V_T$




Simulation

- $V_{DD} = 1.8V$
- $V_N = 1.2V$

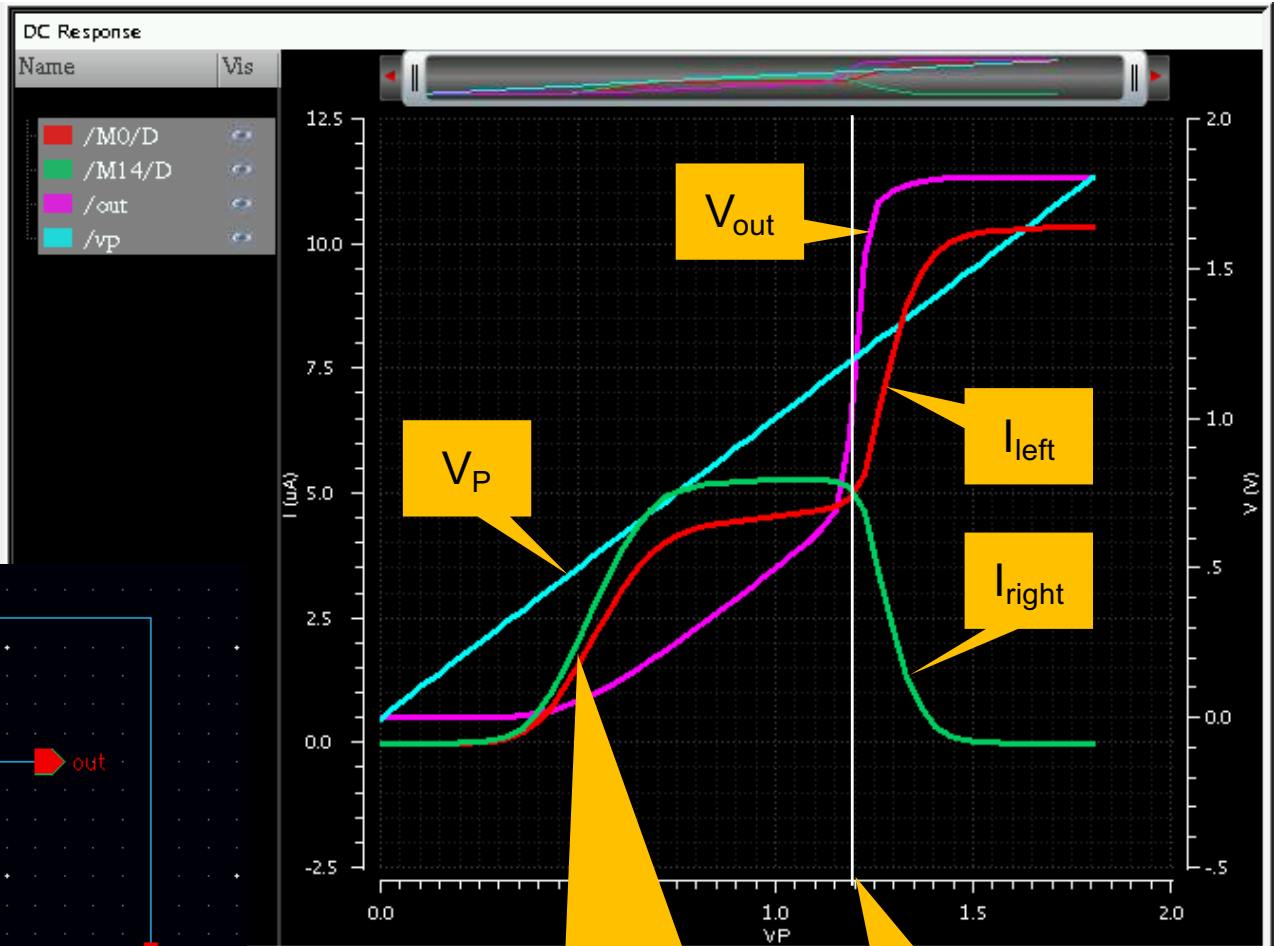

Strange operation here: I_{right} cannot flow because output is low

$V_N = 1.2V$

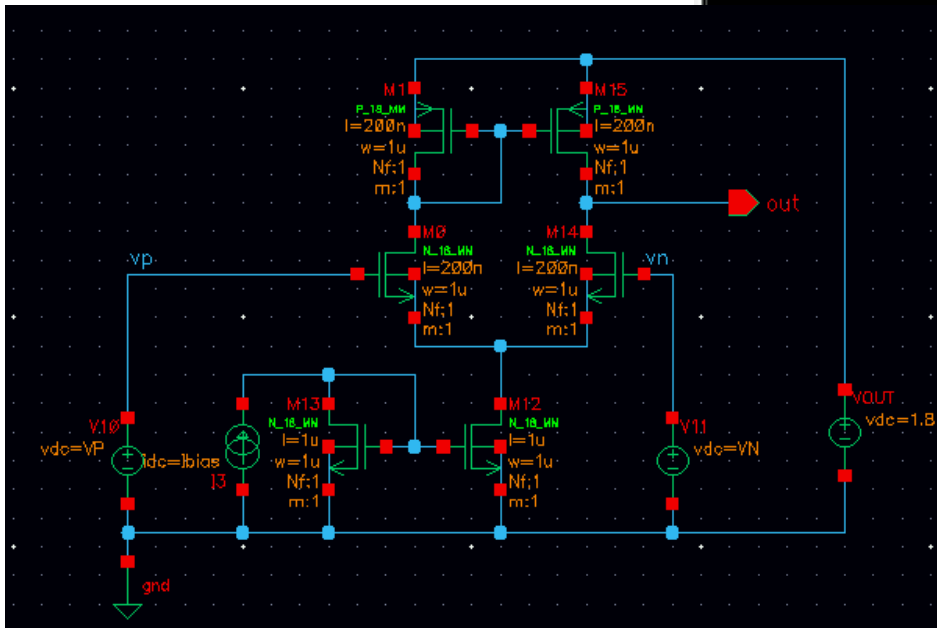




Sweeping V_-

- $V_- = 0.2, 0.4, \dots, 1.6 \text{ V}$

V_{out}

 

For positive V_- ,
the output cannot
go low (lower than V_s)

V_+



Gain

- What is the (voltage) gain?
- To first order, it is – as before – the g_m of the *input* transistor(s) multiplied with the total impedance at the *output* (i.e. r_{ds} of the current mirror output in parallel to r_{ds} of the diff. pair)
- (The output resistance on the left branch do not matter, because the voltage there is kept nearly constant by the diode connected PMOS upper left...)




Comments

- Understanding the large signal behaviour for very different V_p, V_n is important, but in practical circuits, feedback is often applied so that $V_p = V_n$.
- Another important property is the *common mode input range*. This is limited by the V_{GS} of the input pair and the compliance of the tail current source: An *NMOS* differential pair *does not work* any more at *low* (common mode) input voltage.
- Another property is *common mode gain*, i.e. the change in output voltage if both inputs are changes simultaneously. In an ideal amplifier, common mode gain is 0.
- If the amplifier is loaded with a resistive load, gain drops. (as for the gain stage).
 - Therefore a source follower is sometimes added.
 - Stability in feedback circuits is then more tricky. Compensation methods are needed.



More Gain: Diff-Amp with Gain Stage

 - The differential amplifier is often followed by a gain stage
 - This two-stage design has two ,main‘ poles and may need compensation if used in feedback configuration




- The ‘steep’ part of the transfer function of the first (differential) stage should coincide with the ‘steep’ part of the second stage!
- This can be achieved (for 3x equal PMOS) with $I_0 = 2 \times I_1$, so that $I_+ = I_- = I_1$ at the switching point.



Differential Pair + Current Mirror

 - The problem of limited output voltage swing for high input common mode can be solved by mirroring the currents:





Alternative topologies

- Many topologies are possible, using mirrors and cascodes
- For instance this 'folded cascode' configuration

